# 1 HOW THE DC MOTOR WORKS

## 1.1 Task: MAKE DC MORTOT RUN

1. Connect the DC motor to the battery and make it run.
2. You can try different combinations to connect the terminals of the motor like:
    - + and -
    - - and +
    - - and -
    - + and +.

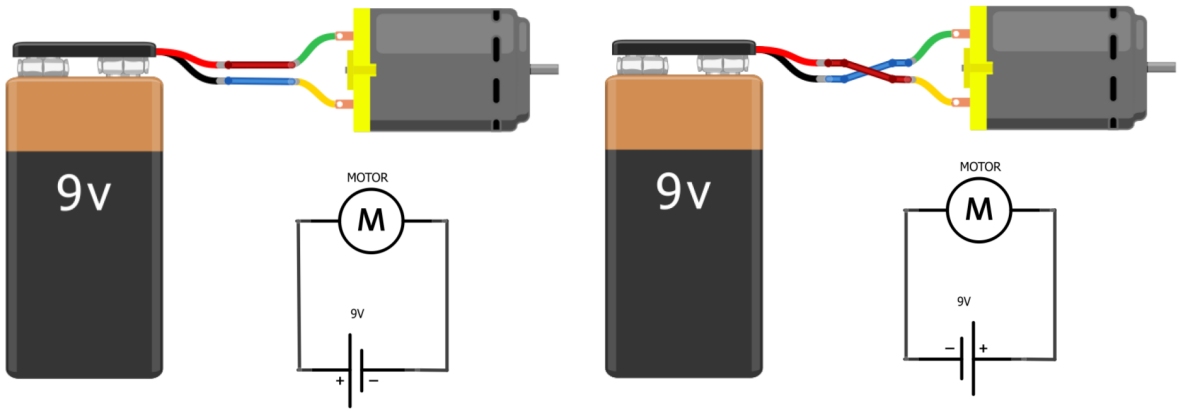


**Figure 1:** DC motor connection.

## 1.2 Questions:

1. In which direction the motor's shaft spins in different situations?
2. In which direction the electric current flow?
3. Why does motor is not spinning when both connectors are connected to + terminal of the battery?

## 1.3 Summary

The rotation of the DC motor depends on the direction of electric current.

## 1.4 Issues

### 1.4.1 *When I connect the DC motor to + and - terminals of the battery the motor's shaft does not spin.*

Check the voltage of the battery… battery may be discharged.
Check the connectors of the motor… may be bad.